

# Concept for the open-rTMS electronics

Tobias Schäfer

1st March 2012

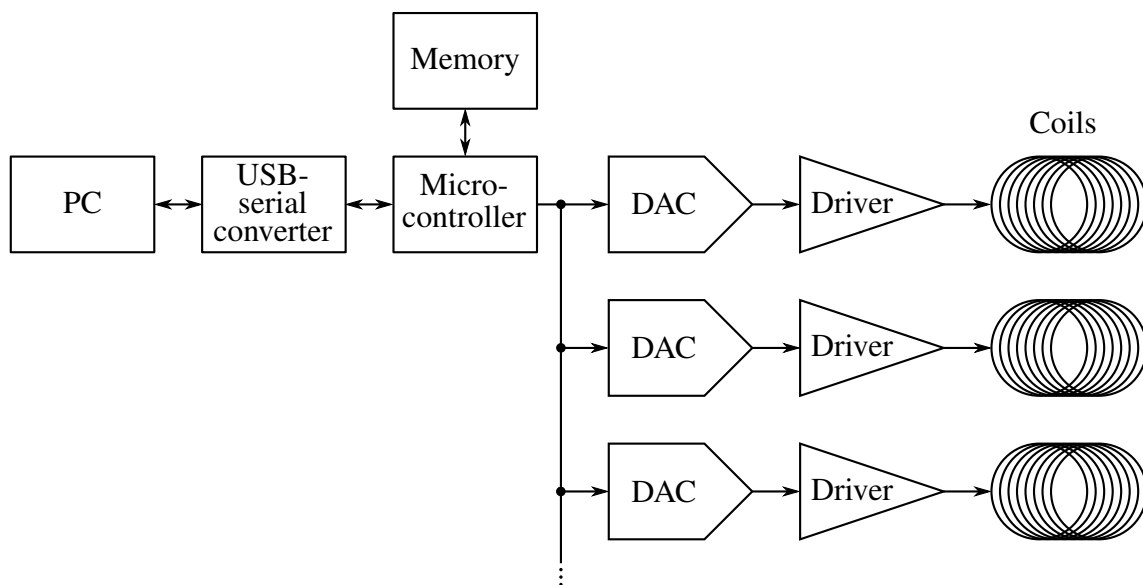


Figure 1: Concept for the system

## Contents

<b>1</b>	<b>Digital part</b>	<b>2</b>
<b>2</b>	<b>Analog part</b>	<b>3</b>
2.1	D/A converter . . . . .	3
2.2	Driver . . . . .	3

# 1 Digital part

Parallax Propeller:

- no programming adapter needed. Communication and programming is done through the serial port.
- available as a discrete part as well as in SMD.
- up to 180 MIPS.
- sinus table in ROM.
- 8 cores.
- 6,95 EURO = 9 USD.

External I2C Memory 24LC256 for program storage (1 EURO = 1.3 USD).

As always: FTDI FT232RL (3.50 EURO = 4.57 USD).

For the Parallax Propeller a starterkit is available (95 Euro = 124 USD). A makeshift TMS device could be made by using the breed board part of the starterkit to assemble the analog part.

## 2 Analog part

### 2.1 D/A converter

Two possibilities:

- Use a pin of the controller to generate a PWM signal and filter the signal.
- Use an external D/A converter.

For the first design I will use a MCP4921 or MCP4922 D/A converter from Microchip.

### 2.2 Driver

Simple current driver made out of two OP-amps. The two OP-amps are necessary, because the voltage supplied via USB is GND to 5 V. One OP-amp is used to generate 2.5 V or more precisely  $V_{ref}/2$ .

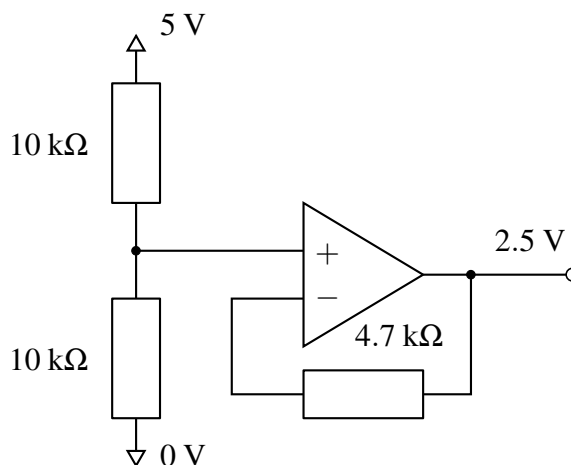


Figure 2: Voltage divider

In case somebody is wondering: The 4.7 kΩ in figure 2 are to make the OP-amp "see" the same impedance on every input pin.

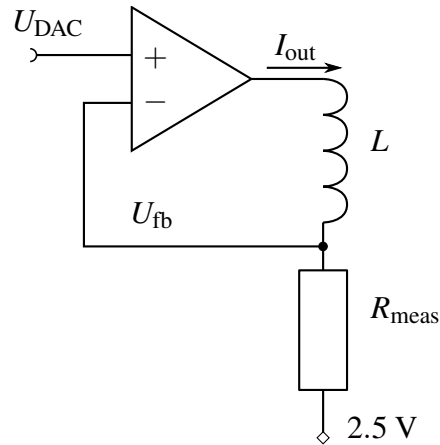


Figure 3: Coil driver

The OP-amp in figure 3 will increase the current  $I_{\text{out}}$  until the feedback voltage  $U_{\text{fb}}$  at the measurement resistor  $R_{\text{meas}}$  matches  $U_{\text{DAC}}$ :

$$U_{\text{DAC}} = I_{\text{out}} \cdot R_{\text{meas}} + 2.5 \text{ V}$$

$$\Leftrightarrow I_{\text{out}} = \frac{U_{\text{DAC}} - 2.5 \text{ V}}{R_{\text{meas}}}$$

For  $R_{\text{meas}} = 100 \Omega$  we get

DAC Value	$U_{\text{DAC}}$	$I_{\text{out}}$
0	0.0 V	-25 mA
1024	1.25 V	-12.5 mA
2048	2.5 V	0 mA
3072	3.75 V	12.5 mA
4095	5.0 V	25 mA

If we use the same voltage as the DAC reference and the input for the voltage divider, the value of 2048 should give a current of precisely 0 mA.